


Q1) A current of 5 A is flowing through a resistor of $15\ \Omega$. Calculate the potential difference between the ends of the resistor. (2)

Q2) Figure (a), (b) and (c) show three cylindrical copper conductors along with their face areas and length. Which of the conductors will have highest resistance and why? (2)

Q3) Resistance of a metal wire of length 1 m is $26\ \Omega$ at 20°C . if the diameter of the wire is 0.3 mm, what will

be the resistivity of the metal at that temperature? (2)

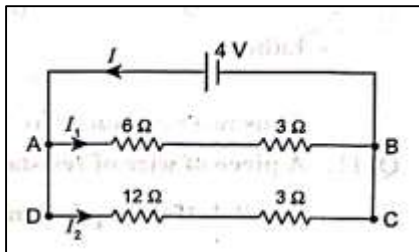Q4) A $4\ \Omega$ resistance wire is doubled on it. Calculate the new resistance of the wire. (3)



Q5) For the circuit shown in the given diagram: what is the value of (i) current through $6\ \Omega$ resistor? (ii) potential difference across $12\ \Omega$ resistor? (3)

Q6) A piece of wire of resistance R is cut into five equal parts. These parts are then connected in parallel. If the equivalent resistance of this combination is R' then find the ratio $\frac{R}{R'}$. (2)

Q7) If in the figure $R_1 = 10\ \Omega$, $R_2 = 40\ \Omega$, $R_3 = 30\ \Omega$, $R_4 = 20\ \Omega$, $R_5 = 60\ \Omega$, and a $12\ \text{V}$ battery is connected to the arrangement, calculate (i) the total resistance in the circuit and (ii) the total current flowing in the circuit. (3)

Q8) What is the commercial unit of electrical energy?


Represent it in terms of joules. (2)

Q9) Two resistance of $4\ \Omega$ and $6\ \Omega$ are connected in parallel. The combination is connected across a $6\ \text{V}$ battery of negligible resistance. Calculate (i) the power supplied by the battery (ii) the power dissipated in each resistor. (3)

Q10) An electric bulb is rated $220\ \text{V}$ and $100\ \text{W}$. calculate the power consumed when it is operated on $110\ \text{V}$. (2)

Q11) Two conducting wires of the same material and of equal length and equal diameters are first connected in series and then in parallel in a circuit across the same potential difference. Find the ratio of heat produced in series and parallel combination. (3)

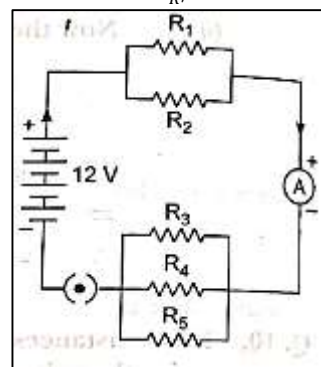
Q12) A heater coil is rated $100\ \text{W}$, $200\ \text{V}$. if it is cut into two identical parts. Both parts are connected together in parallel to the same source of $200\ \text{V}$. calculate the energy liberated per second in the new combination. (3)




Q1) A current of 5 A is flowing through a resistor of $15\ \Omega$. Calculate the potential difference between the ends of the resistor. (2)

Q2) Figure (a), (b) and (c) show three cylindrical copper conductors along with their face areas and length. Which of the conductors will have highest resistance and why? (2)

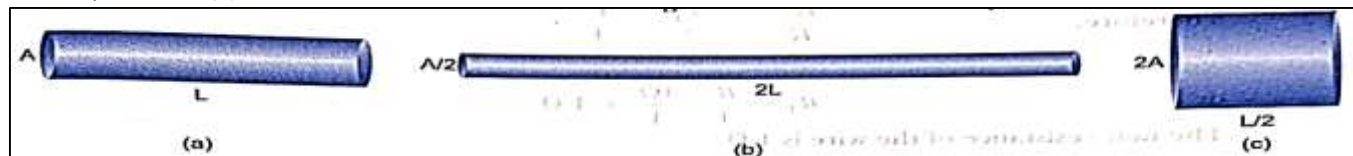Q3) Resistance of a metal wire of length 1 m is $26\ \Omega$ at 20°C . if the diameter of the wire is 0.3 mm, what will be the resistivity of the metal at that temperature? (2)



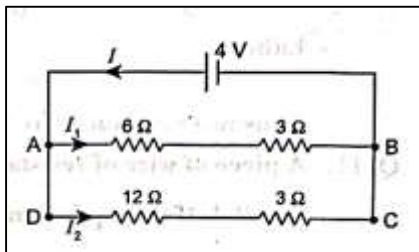Q4) A $4\ \Omega$ resistance wire is doubled on it. Calculate the new resistance of the wire. (3)



Q5) For the circuit shown in the given diagram: what is the value of (i) current through $6\ \Omega$ resistor? (ii) potential difference across $12\ \Omega$ resistor? (3)

Q6) A piece of wire of resistance R is cut into five equal parts. These parts are then connected in parallel. If the equivalent resistance of this combination is R' then find the ratio $\frac{R}{R'}$. (2)

Q7) If in the figure $R_1 = 10\ \Omega$, $R_2 = 40\ \Omega$, $R_3 = 30\ \Omega$, $R_4 = 20\ \Omega$, $R_5 = 60\ \Omega$, and a $12\ \text{V}$ battery is connected to the arrangement, calculate (i) the total resistance in the circuit and (ii) the total current flowing in the circuit. (3)

Q8) What is the commercial unit of electrical energy?

Represent it in terms of joules. (2)

Q9) Two resistance of $4\ \Omega$ and $6\ \Omega$ are connected in parallel. The combination is connected across a $6\ \text{V}$ battery of negligible resistance. Calculate (i) the power supplied by the battery (ii) the power dissipated in each resistor. (3)

Q10) An electric bulb is rated $220\ \text{V}$ and $100\ \text{W}$. calculate the power consumed when it is operated on $110\ \text{V}$. (2)

Q11) Two conducting wires of the same material and of equal length and equal diameters are first connected in series and then in parallel in a circuit across the same potential difference. Find the ratio of heat produced in series and parallel combination. (3)

Q12) A heater coil is rated $100\ \text{W}$, $200\ \text{V}$. if it is cut into two identical parts. Both parts are connected together in parallel to the same source of $200\ \text{V}$. calculate the energy liberated per second in the new combination. (3)

